

## Lab 2

Milen Dimitrov

(Lecture 5/6)

FPGA Verilog

1. Install ModelSim
2. Design a 2 bit adder
3. Simulate a 2-bit adder in ModelSim.
4. Submit a single PDF file that contains the Verilog code and a screenshot of the output.

Designing and implementing 4bit adder by different modeling strategies:

# 1. Gate Level Modeling

adder.v

```
`timescale 1ns/1ps
module adder (s,cout,a,b);
    input [3:0] a;
    input [3:0] b;
    output [3:0] s;
    output cout;
    wire [2:0] carry;

    half_adder a0(s[0],carry[0],a[0],b[0]);
    full_adder a1(s[1],carry[1],a[1],b[1],carry[0]);
    full_adder a2(s[2],carry[2],a[2],b[2],carry[1]);
    full_adder a3(s[3],cout,a[3],b[3],carry[2]);

endmodule
//=====
module half_adder (s,cout,a,b);
    input a;
    input b;
    output s;
    output cout;
    xor(s,a,b);
    and(cout,a,b);
endmodule
//=====
module full_adder(s,cout,a,b,cin);
```

```
input a;
input b;
input cin;
output s;
output cout;
wire i1,i2,i3;
  xor (i1,a,b);
  and (i2,a,b);
  xor (s,i1,cin);
  and (i3,i1,cin);
  or (cout,i2,i3);
endmodule
```

tb\_adder.v

```
`timescale 1ns/1ps
module tb_adder ();

  reg [3:0] a,b;
  wire [3:0] s;
  wire cout;

  initial  for (a=0;a<18;a=a+1) #180 ;

  initial  for (b=0;b<18;b=b+1) #10 ;

  adder test_adder(s,cout,a,b);
endmodule
```

ModelSim - INTEL FPGA STARTER EDITION 10.5b

File Edit View Compile Simulate Add Source Tools Layout Bookmarks Window Help

100 ps

Layout Simulate ColumnLayout [AllCo]

sim - Default

| Instance        | Design unit | Design unit type | Top Category |
|-----------------|-------------|------------------|--------------|
| tb_adder        | tb_adder    | Module           | DU Instance  |
| test_adder      | adder       | Module           | DU Instance  |
| #INITIAL#8      | tb_adder    | Process          | -            |
| #INITIAL#10     | tb_adder    | Process          | -            |
| #vsim_capacity# | Capacity    | Statistics       | -            |

Objects

| Name  | Value | Kind | Mode     |
|-------|-------|------|----------|
| a     | 0100  | Net  | In       |
| b     | 1000  | Net  | In       |
| s     | 1100  | Net  | Out      |
| cout  | S'0   | Net  | Out      |
| carry | 000   | Net  | Internal |

Processes (Active)

| Name | Type (filtered) | State | Order | Parent Path |
|------|-----------------|-------|-------|-------------|
|------|-----------------|-------|-------|-------------|

Ln#

```

1 timescale 1ns/1ps
2 module adder (s,cout,a,b);
3   input [3:0] a;
4   input [3:0] b;
5   output [3:0] s;
6   output cout;
7   wire [2:0] carry;
8
9   half_adder a0(s[0],carry[0],a[0],b[0]);
10  full_adder a1(s[1],carry[1],a[1],b[1],carry[0]);
11  full_adder a2(s[2],carry[2],a[2],b[2],carry[1]);
12  full_adder a3(s[3],cout ,a[3],b[3],carry[2]);
13
14 endmodule
15 //=====
16 module half_adder (s,cout,a,b);
17   input a;
18   input b;
19   output s;
20   output cout;
21   xor(s,a,b);
22   and(cout,a,b);
23 endmodule
24 //=====
25 module full_adder(s,cout,a,b,cin);
26   input a;
27   input b;
28   input cin;
29   output s;
30   output cout;
31   wire i1,i2,i3;
32   xor(i1,a,b);
33   and(i2,a,b);
34   xor(s,i1,cin);
35   and(i3,i1,cin);
36   or(cout,i2,i3);
37 endmodule
38
39
40

```

Wave

adder.v tb\_adder.v \*

Transcript

```

VSI91> vsim work.tb_adder
# End time: 23:35:28 on May 10, 2022, Elapsed time: 0:02:20
# Errors: 0, Warnings: 0
# vsim work.tb_adder
# Start time: 23:35:28 on May 10, 2022
# Loading work.tb_adder
# Loading work.adder
# Loading work.half_adder
# Loading work.full_adder
add wave -position insertpoint sim://tb_adder/test_adder/*
VSI93> run 3600000
VSI94>

```

File Edit View Compile Simulate Add Structure Tools Layout Bookmarks Window Help

100 ps

Layout Simulate ColumnLayout [AllCo]

sim - Default

| Instance        | Design unit | Design unit type | Top Category |
|-----------------|-------------|------------------|--------------|
| tb_adder        | tb_adder    | Module           | DU Instance  |
| test_adder      | adder       | Module           | DU Instance  |
| a0              | half_adder  | Module           | DU Instance  |
| a1              | full_adder  | Module           | DU Instance  |
| a2              | full_adder  | Module           | DU Instance  |
| a3              | full_adder  | Module           | DU Instance  |
| #INITIAL#8      | tb_adder    | Process          | -            |
| #INITIAL#10     | tb_adder    | Process          | -            |
| #vsim_capacity# | Capacity    | Statistics       | -            |

Objects






| Name  | Value | Kind | Mode     |
|-------|-------|------|----------|
| a     | 0100  | Net  | In       |
| b     | 1000  | Net  | In       |
| s     | 1100  | Net  | Out      |
| cout  | S'0   | Net  | Out      |
| carry | 000   | Net  | Internal |

Ln#

```

1 timescale 1ns/1ps
2 module tb_adder ();
3
4   reg [3:0] a,b;
5   wire [3:0] s;
6   wire cout;
7
8   initial for (a=0;a<18;a=a+1) #180 ;
9
10  initial for (b=0;b<18;b=b+1) #10 ;
11
12  adder test_adder(s,cout,a,b);
13 endmodule
14

```

     

## 2. Data Flow Modeling



adder\_data.v

```
`timescale 1ns/1ps
module adder_data (s,cout,a,b);
    input [3:0] a;
    input [3:0] b;
    output [3:0] s;
    output cout;
    wire [2:0] carry;

    half_adder_data a0(s[0],carry[0],a[0],b[0]);
    full_adder_data a1(s[1],carry[1],a[1],b[1],carry[0]);
    full_adder_data a2(s[2],carry[2],a[2],b[2],carry[1]);
    full_adder_data a3(s[3],cout,a[3],b[3],carry[2]);

endmodule
```

```
//=====
module half_adder_data (s,cout,a,b);
    input a;
    input b;
    output s;
    output cout;
    assign s=a^b;
    assign cout=a&b;
endmodule
//=====
module full_adder_data(s,cout,a,b,cin);
    input a;
    input b;
    input cin;
    output s;
    output cout;
    wire i1,i2,i3;
    assign s=i1^cin;
    assign i2=a&b;
    assign i1=a^b;
    assign i3=cin&i1;
    assign cout=i2|i3;
endmodule
```

  

### 3. Behavioral Modeling

adder\_beh.v


```
`timescale 1ns/1ps
module adder_beh (s,cout,a,b);
    input [3:0] a;
    input [3:0] b;
    output [3:0] s;
    output cout;
    wire [2:0] carry;


    half_adder_beh a0(s[0],carry[0],a[0],b[0]);
    full_adder_beh a1(s[1],carry[1],a[1],b[1],carry[0]);
    full_adder_beh a2(s[2],carry[2],a[2],b[2],carry[1]);
    full_adder_beh a3(s[3],cout,a[3],b[3],carry[2]);
```

```

endmodule
//=====
module half_adder_beh (s,cout,a,b);
    input a;
    input b;
    output s;
    output cout;
    reg s,cout;
    always@(a,b)
    begin
        if (a==b)
            begin
                s=0;
                cout=b;
            end
        else
            begin
                s=1;
                cout=0;
            end
        end
    end
endmodule
//=====
module full_adder_beh (s,cout,a,b,cin);
    input a;
    input b;
    input cin;
    output s;
    output cout;
    reg s,cout;
    always@(a,b,cin)
    begin
        if (a==b)
            begin
                s=cin;
                cout=b;
            end
        else
            begin
                s=~cin;
                cout=cin;
            end
        end
    end
endmodule



```

 


 


## 4. Running it in Vivado:

Same waveform in Vivado simulator

 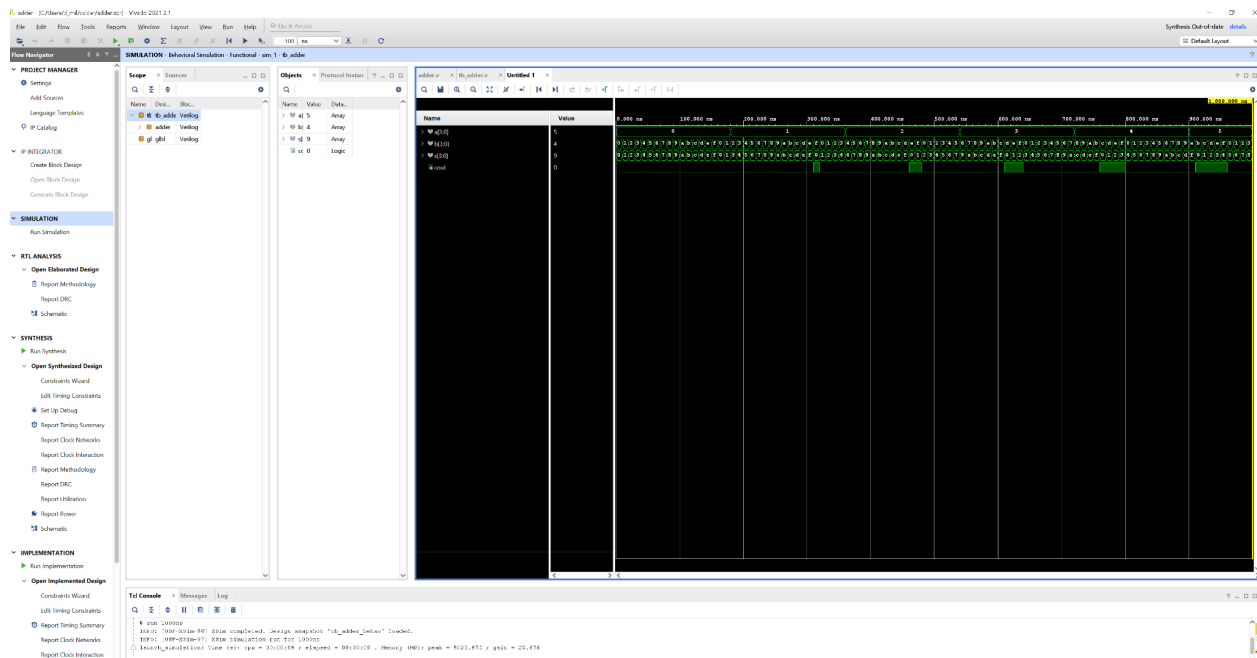


## 5. Schematics in Vivado :

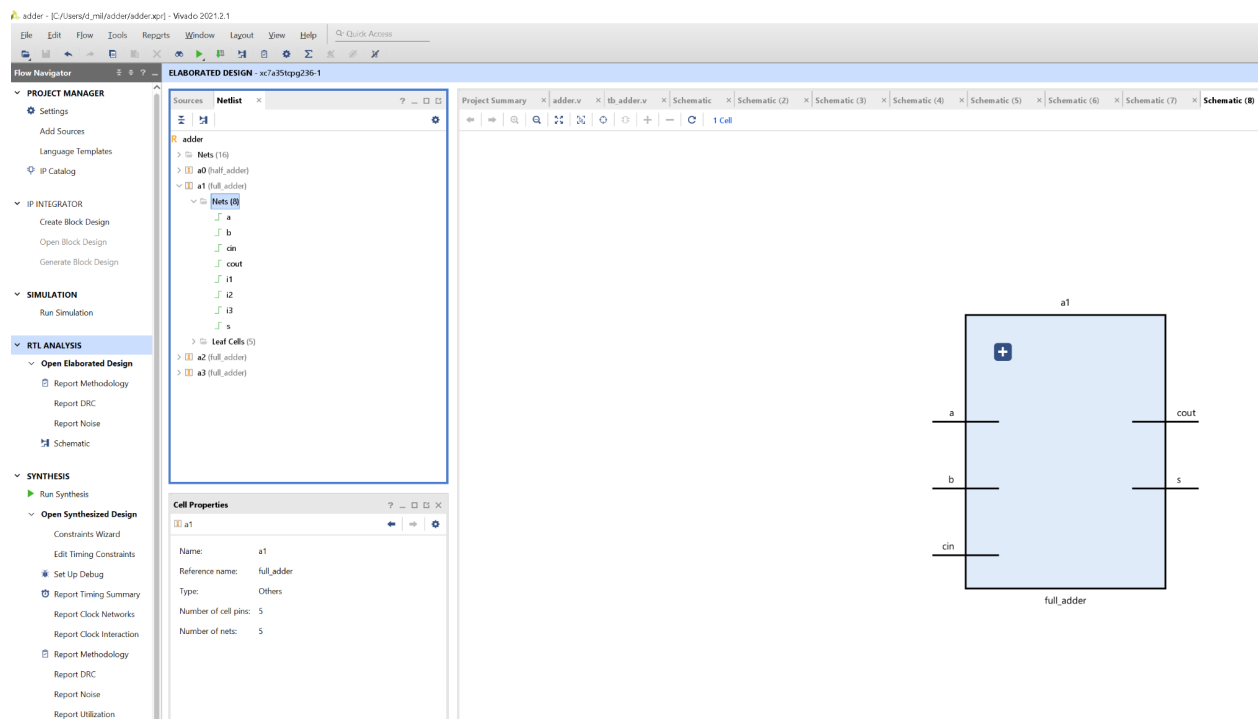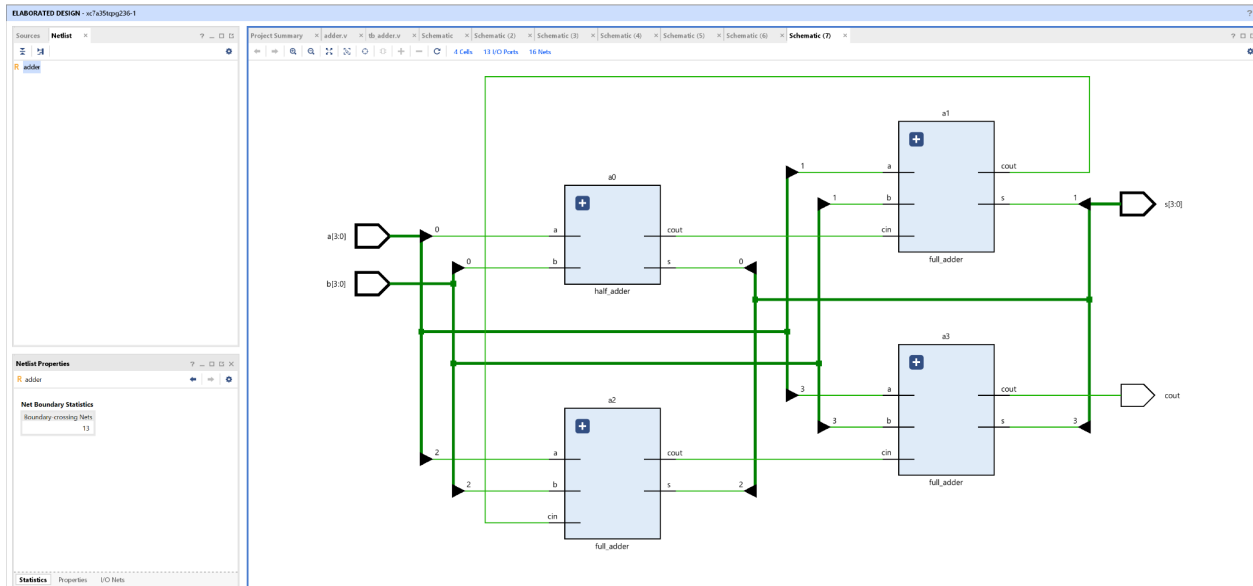



## 6. Synthesized design in Vivado:

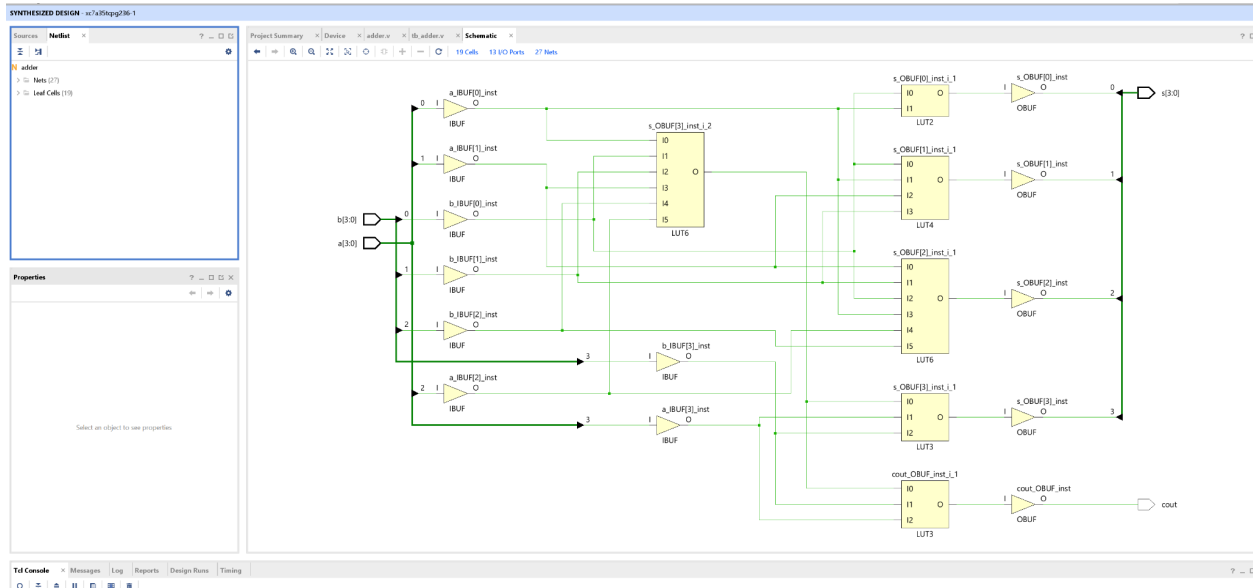

## 7. Generated bitstream and programed the FPGA

Constrains File:

```
set_property PACKAGE_PIN V17 [get_ports {a[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {a[0]}]
set_property PACKAGE_PIN V16 [get_ports {a[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {a[1]}]
set_property PACKAGE_PIN W16 [get_ports {a[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {a[2]}]
set_property PACKAGE_PIN W17 [get_ports {a[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {a[3]}]
set_property PACKAGE_PIN W15 [get_ports {b[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {b[0]}]
set_property PACKAGE_PIN V15 [get_ports {b[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {b[1]}]
set_property PACKAGE_PIN W14 [get_ports {b[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {b[2]}]
set_property PACKAGE_PIN W13 [get_ports {b[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {b[3]}]
set_property PACKAGE_PIN V2 [get_ports {sw[8]}]

## LEDs
set_property PACKAGE_PIN U16 [get_ports {s[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {s[0]}]
set_property PACKAGE_PIN E19 [get_ports {s[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {s[1]}]
```

```
set_property PACKAGE_PIN U19 [get_ports {s[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {s[2]}]
set_property PACKAGE_PIN V19 [get_ports {s[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {s[3]}]
set_property PACKAGE_PIN W18 [get_ports {cout}]
    set_property IOSTANDARD LVCMOS33 [get_ports {cout}]
```

